

Lab Assessment Rubrics of Digital System Design (CPE-344)										
Lab Number			11							
Lab Title			Implementation of 4 bit shift register and majority counter							
Submitted by										
Names			Registration Number							
Sumaira Safeer			FA22-BCE-019							
Rubrics name & number							Marks			
							In-Lab		Post-Lab	
Engineering Knowledge	R2: Use of Engineering Knowledge and follow Experiment Procedures: <i>Ability to follow experimental procedures, control variables, and record procedural steps on lab report.</i>									
	R3: Interpretation of Subject Knowledge: <i>Ability to interpret and explain mathematical and/or visual forms, including equations, diagrams, graphics, figures, and tables.</i>									
Problem Analysis	R6: Experimental Data Analysis: <i>Ability to interpret findings, compare them to values in the literature, identify weaknesses and limitations.</i>									
Design	R7: Implementing Design Strategy: <i>Ability to execute a solution taking into consideration design requirements and pertinent contextual elements. [Block Diagram/Flow chart/Circuit Diagram]</i>									
	R8: Best Coding Standards: <i>Ability to follow the coding standards and programming practices.</i>									
Modern Tools Usage	R9: Understand Tools: <i>Ability to describe and explain the principles behind and applicability of engineering tools.</i>									
	R11: Tools Evaluation: <i>Ability to simulate the experiment and them using hardware tools to verify The results.</i>									
Individual and Teamwork	R12: Individual Work Contributions: <i>Ability to carry out individual responsibilities.</i>									
	R13: Management of Teamwork: <i>Ability to appreciate, understand and work with multidisciplinary team members.</i>									
Rubrics to follow										
Rubrics	R2	R3	R5	R6	R7	R8	R9	R11	R12	R13
In-Lab										
Post-Lab										

Lab: 11

1. Objectives:

The objective of this lab is to get familiar with

- Implementation of Task in Verilog
- Implementation of Function in Verilog

2. Lab Tasks:

2.1. Task#01:

Alu Designing using Task

Solution:

- Verilog Code

```
module aluUsingTask(func, a, b, c);

    input [1:0]func;
    input [3:0]a, b;
    output [3:0]c;
    reg[3:0]c;

    task my_and;
        input [3:0]a, b;
        output [3:0]andout;
        integer i;

        begin
            for (i =3; i>=0; i= i-1)
                andout[i]=a[i]&b[i];
            end
        endtask

    always@(func or a or b)
        begin
            case(func)
                2'b00:my_and(a, b, c);
                2'b01:c=a|b;
                2'b10: c=a-b;
                default: c=a+b;
            endcase
        end

endmodule
```

- **Verilog Test Bench**

```
module aluTestBench;

    // Inputs
    reg [1:0] func;
    reg [3:0] a;
    reg [3:0] b;

    // Outputs
    wire [3:0] c;

    // Instantiate the Unit Under Test (UUT)
    aluUsingTask uut (
        .func(func),
        .a(a),
        .b(b),
        .c(c)
    );

    initial begin
        // Initialize Inputs
        func = 0;
        a = 0;
        b = 0;

        // Wait 100 ns for global reset to finish
        #100;

        // Add stimulus here
        // Initialize Inputs
        func = 1;
        a = 0;
        b = 0;

        // Wait 100 ns for global reset to finish
        #100;

        // Add stimulus here
        // Initialize Inputs
        func = 1;
        a = 0;
        b = 1;
    end
endmodule
```

```

// Wait 100 ns for global reset to finish
#100;

// Add stimulus here
func = 1;
a = 1;
b = 0;

// Wait 100 ns for global reset to finish
#100;

// Add stimulus here
func = 1;
a = 1;
b = 1;


// Wait 100 ns for global reset to finish
#100;

end


endmodule

```

- Waveform

 

- RTL Diagram

 

2.2. Task#02:

Designing RCA using task

Solution:

- **Verilog Code**

```
module rcaUsingTask(input wire[3:0] a, input wire[3:0] b, input wire c_in, output
reg c_out, output reg [3:0] sum);
reg carry[4:0];
integer i;

task FA(input in1, input in2, input carry_in, output reg out, output carry_out);
{carry_out, out} = in1 + in2 + carry_in;
endtask

always @(*)
begin
carry[0] = c_in;
for(i = 0; i<4; i= i+1)
begin
FA (a[i], b[i], carry [i], sum[i], carry[i+1]);
end
c_out = carry [4];
end

endmodule
```

- **Verilog Test Bench**

```
module rcaTestBenchUsingTask;

// Inputs
reg [3:0] a;
reg [3:0] b;
reg c_in;

// Outputs
wire c_out;
wire [3:0] sum;
```

```

// Instantiate the Unit Under Test (UUT)
rcaUsingTask uut (
    .a(a),
    .b(b),
    .c_in(c_in),
    .c_out(c_out),
    .sum(sum)
);

initial begin
    // Initialize Inputs
    a = 0;
    b = 0;
    c_in = 0;

    // Wait 100 ns for global reset to finish
    #100;

    // Add stimulus here
    // Initialize Inputs
    a = 0;
    b = 1;
    c_in = 1;

    // Wait 100 ns for global reset to finish
    #100;
    // Initialize Inputs
    a = 1;
    b = 0;
    c_in = 1;

    // Wait 100 ns for global reset to finish
    #100;
    // Initialize Inputs
    a = 1;
    b = 1;
    c_in = 1;

    // Wait 100 ns for global reset to finish
    #100;
    // Initialize Inputs
    a = 1;

```

```


        b = 1;
        c_in = 0;

        // Wait 100 ns for global reset to finish
        #100;
        // Initialize Inputs
        a = 0;
        b = 1;
        c_in = 0;


    end
endmodule

```

- Waveform

 

- RTL Diagram

 

2.3. Task#03

Design 4x1 using 2x1 function

Solution:

- **Verilog Code**

```
module MUX4to1(input [3:0] in, input [1:0] sel, output out);
    wire out1, out2;

    function MUX2to1;
        input in1, in2;
        input select;
        MUX2to1 = select ? in2:in1;
    endfunction

    assign out1 = MUX2to1(in[0], in[1], sel[0]);
    assign out2= MUX2to1(in[2], in[3], sel[0]);
    assign out= MUX2to1(out1, out2, sel[1]);

endmodule
```

- **Verilog Test Bench**

```
module muxUsingFunction;
    // Inputs
    reg [3:0] in;
    reg [1:0] sel;

    // Outputs
    wire out;

    // Instantiate the Unit Under Test (UUT)
    MUX4to1 uut (
        .in(in),
        .sel(sel),
        .out(out)
    );

    initial begin
        // Initialize Inputs
        in = 4'b0001;
        sel = 2'b00;

        // Wait 100 ns for global reset to finish
        #100;

        // Add stimulus here
    end
endmodule
```



```

        in = 4'b0010;
        sel = 2'b01;

        // Wait 100 ns for global reset to finish
        #100;
        // Initialize Inputs
        in = 4'b0100;
        sel = 2'b10;

        // Wait 100 ns for global reset to finish
        #100;
        // Initialize Inputs
        in = 4'b1000;
        sel = 2'b11;


        // Wait 100 ns for global reset to finish
        #100;

    end


endmodule

```

- **Waveform**

 

- **RTL Diagram**

 

2.4. Post Lab Task#01

64 Bit Comparator Using 8 Bit with Task

Solution:

- Verilog Code**

```

module Compareator();
input [63:0]Num1,Num2;
output Greater,Equaler,Lesser;
wire [7:0]G,E,L;
wire [5:0]Great,Equal,Less;
//////////TASK//////////
task Compare;
input wire [7:0]A,B;
output reg G,E,L;
begin
if(A>B)
begin
G = 1'b1; L = 1'b0; E = 1'b0;
end
else if(A<B)
begin
G = 1'b0;L = 1'b1;E = 1'b0;
end
else
begin

```

```

G = 1'b0; L = 1'b0; E = 1'b1;
end
end
endtask
Compare(Num1[7:0],Num2[7:0],G[0],E[0],L[0]);
Compare(Num1[15:8],Num2[15:8],G[1],E[1],L[1]);
Compare(Num1[23:16],Num2[23:16],G[2],E[2],L[2]);
Compare(Num1[31:24],Num2[31:24],G[3],E[3],L[3]);
Compare(Num1[39:32],Num2[39:32],G[4],E[4],L[4]);
Compare(Num1[47:40],Num2[47:40],G[5],E[5],L[5]);
Compare(Num1[55:48],Num2[55:48],G[6],E[6],L[6]);
Compare(Num1[63:56],Num2[63:56],G[7],E[7],L[7]);
// Creation Of 16 Bit Result
assign Equal[0]=E[0]&E[1];
assign Equal[1]=E[2]&E[3];
assign Equal[2]=E[4]&E[5];
assign Equal[3]=E[6]&E[7];
assign Great[0]=(E[1]&G[0])|G[1];
assign Great[1]=(E[3]&G[2])|G[3];
assign Great[2]=(E[5]&G[4])|G[5];
assign Great[3]=(E[7]&G[6])|G[7];
assign Less[0]=(E[1]&L[0])|L[1];
assign Less[1]=(E[3]&L[2])|L[3];
assign Less[2]=(E[5]&L[4])|L[5];
assign Less[3]=(E[7]&L[6])|L[7];
//Creation Of 32 Bit Results
assign Equal[4]=Equal[0]&Equal[1];
assign Equal[5]=Equal[2]&Equal[3];
assign Great[4]=(Equal[1]&Great[0])|Great[1];
assign Great[5]=(Equal[3]&Great[2])|Great[3];
assign Less[4]=(Equal[1]&Less[0])|Less[1];
assign Less[5]=(Equal[3]&Less[2])|Less[3];
//Creation Of 64 Bit Results
assign Equaler = Equal[4]&Equal[5];
assign Greater= (Equal[5]&Great[4])|Great[5];
assign Lesser= (Equal[5]&Less[4])|Less[5];
endmodule

```

- **Verilog Test Bench**


```

module testBench;
    reg [63:0] Num1;
    reg [63:0] Num2;

```

[illegible]

- **Waveform**

 

- **RTL Diagram**

